### 7-Segment Display using VAMAN

B603 Lab

Indian Institute of Technology, Hyderabad.

December 11, 2021




### Components

- Vaman
- 2 7447 IC
- 3 7 Segment Display




## Pinout Diagram of 7-Segment Display

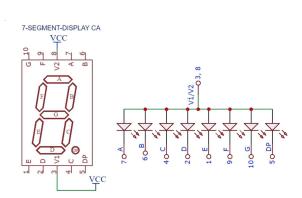




#### Flow Chart:

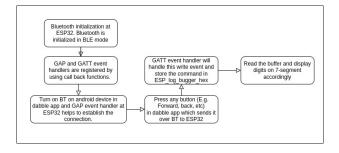

# Wiring Diagram:

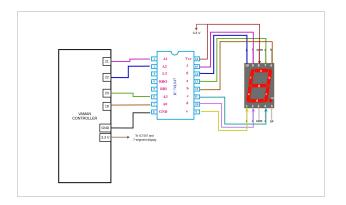

#### Code

Flash the code to Vaman. https://github.com/AnilMondedla/Vaman/blob/main/ Vaman\_spi/main/hello\_world\_main.c

